

# 1. Equation of the RC Circuit.

$$RC \frac{dV_c}{dt} + V_c = V_i$$

$$RCs V_c(s) + V_c(s) = V_i(s)$$

$$\therefore \frac{V_c(s)}{V_i(s)} = \frac{1}{RCs+1} = \frac{1}{\frac{s}{\frac{1}{RC}} + 1}$$

$$R = 1k\Omega, C = 0.1\mu F \quad RC = 10^{-4}$$


$$\therefore H(s) = \frac{1}{\frac{s}{10^4} + 1}$$

break point frequency is  $10^4$  rad/sec

Bode plot:

$$k = 1$$

$$20 \log k = 0$$

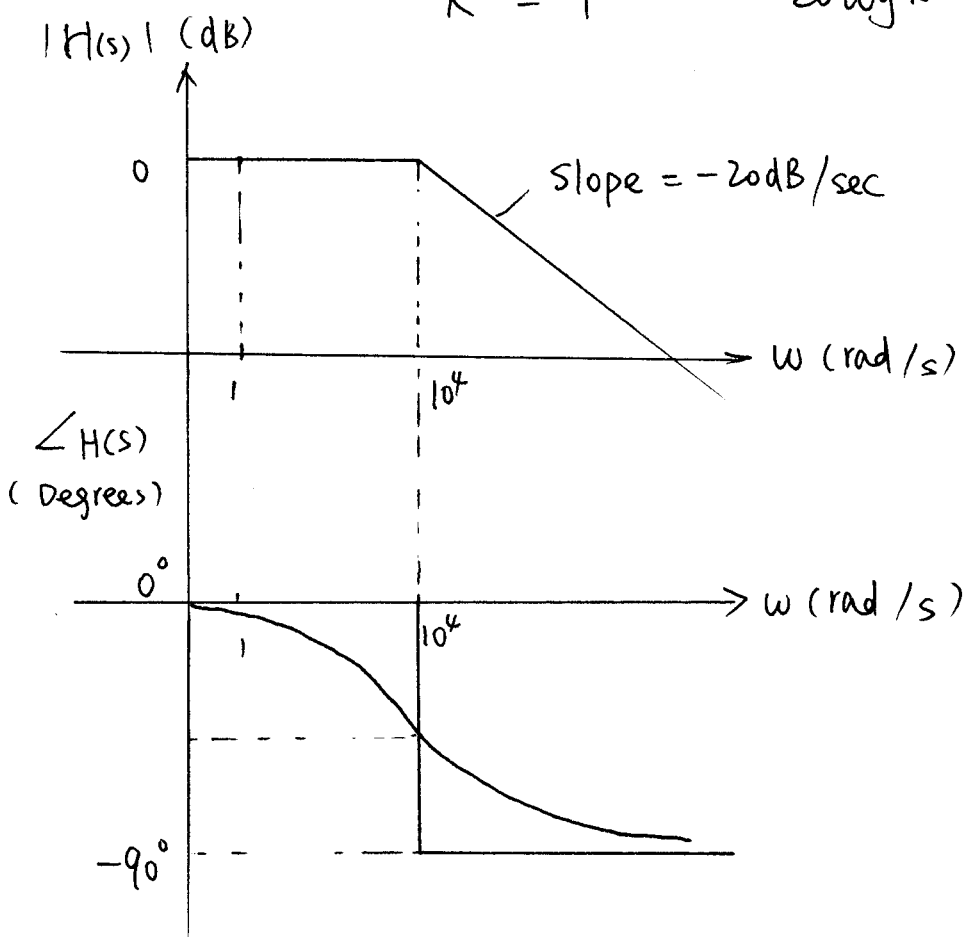

## 2. Equation of RC band-pass filter

$$\int C_1 \frac{dV_C}{dt} = \frac{V_2}{R_2} + C_2 \frac{dV_{C_2}}{dt} \quad (1)$$

$$\int V_{C_2} + V_{C_1} + R_1 C_1 \frac{dV_{C_1}}{dt} = V_1 \quad (2)$$

$$(1) \Rightarrow R_2 s C_1 V_{C_1}(s) = V_{C_2}(s) + s R_2 C_2 V_{C_2}(s)$$

$$\Rightarrow V_{C_1} = \frac{1 + s R_2 C_2}{R_2 s C_1} V_{C_2} \quad (3)$$

$$(2), (3) \Rightarrow V_{C_2}(s) + \frac{1 + s R_2 C_2}{R_2 s C_1} V_{C_2}(s) + R_1 C_1 s \cdot V_{C_2}(s) \frac{1 + s R_2 C_2}{R_2 s C_1} = V_1(s)$$

$$\left[ 1 + \frac{1 + s R_2 C_2}{R_2 s C_1} + \frac{R_1}{R_2} (1 + s R_2 C_2) \right] V_{C_2}(s) = V_1(s)$$

$$\begin{aligned} \therefore H(s) &= \frac{V_{C_2}(s)}{V_1(s)} = \frac{R_2 s C_1}{R_2 s C_1 + 1 + s R_2 C_2 + s C_1 R_1 (1 + s R_2 C_2)} \\ &= \frac{R_2 s C_1}{s^2 R_1 R_2 C_1 C_2 + s(R_1 C_1 + R_2 C_2 + R_2 C_1) + 1} \end{aligned}$$


$$R_1 = R_2 = 1 \text{ k}\Omega, \quad C_1 = C_2 = 10^{-7} \text{ F}$$

$$\therefore H(s) = \frac{10^{-4} \cdot s}{\frac{s^2}{10^8} + \frac{s}{\frac{1}{3} \times 10^4} + 1} = \frac{10^{-4} \cdot s}{\frac{s^2}{10^8} + \frac{s}{\frac{10^4}{3}} + 1}$$

$\therefore$  break point frequency is  $10^4$  rad/sec.

$$k = 10^{-4} \quad 20 \log k = -80 \text{ dB}$$

Bode plot:

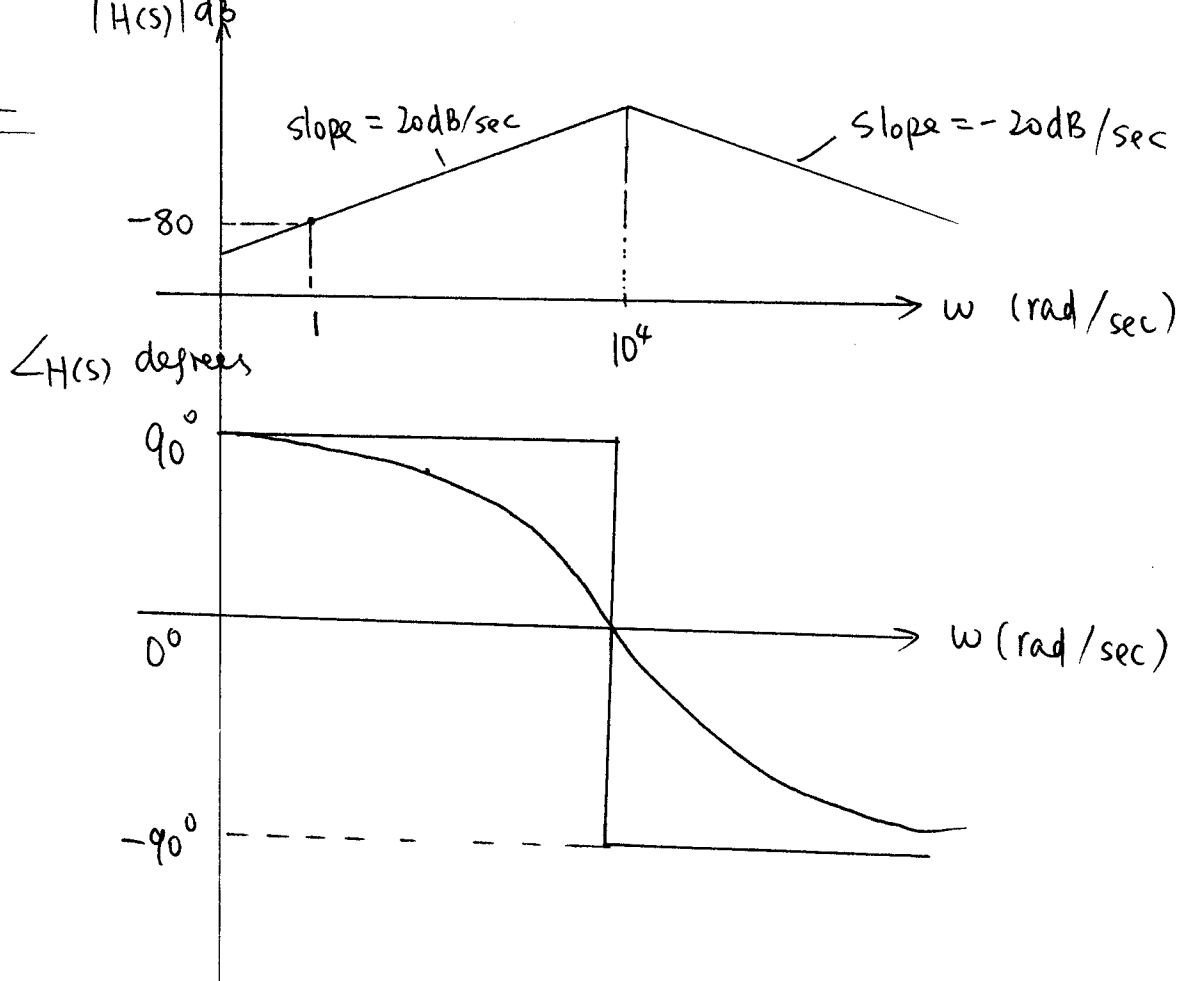

3. Equation of RLC Circuit

$$V_{in} = L \cdot \frac{di_L}{dt} + V_o \quad (1)$$

$$i_L = \frac{V_o}{R} + C \frac{dV_o}{dt} \quad (2)$$

$$(1) \Rightarrow V_{in}(s) = sL \bar{i}_L(s) + V_o(s) \quad (3)$$

$$(2) \Rightarrow \bar{i}_L(s) = \frac{V_o(s)}{R} + sC V_o(s) \quad (4)$$

$$(3) \rightarrow (4) \Rightarrow V_{in}(s) = LS \left( \frac{V_o(s)}{R} + sC V_o(s) \right) + V_o(s)$$

$$= \left( \frac{L}{R} s + L C s^2 + 1 \right) V_o(s)$$

$$\therefore H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1}{\frac{s}{\frac{R}{L}} + \frac{s^2}{\frac{1}{LC}} + 1}$$

$$C = 10^{-7} \text{ F}, \quad R = 10^3 \Omega, \quad L = 0.4 \text{ H}$$

$$\therefore H(s) = \frac{1}{\frac{s^2}{\frac{10^8}{4}} + \frac{s}{\frac{10^4}{4}} + 1}$$

$\therefore$  break point frequency is  $\frac{10^4}{2} = 5 \times 10^3 \text{ rad/sec}$

$$k = 1 \quad 20 \log k = 0$$

Bode plot:

